

# Introduction to Capacitor Circuits

( Tom Co 2/14/2008)

## I. Capacitors

### Basics:

#### 1. Components:

- a. Two conducting plates
- b. Dielectric material (e.g. ceramic, air, etc.) Figure 1

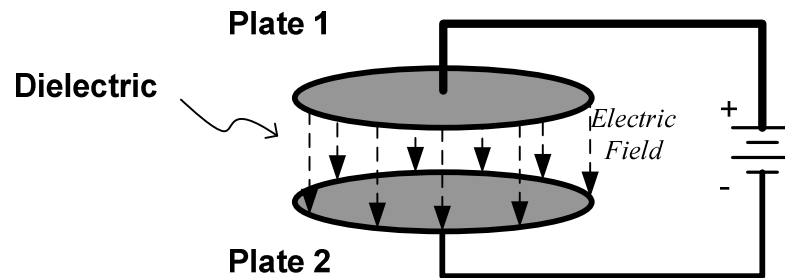


Figure 1. Capacitor charging configuration.

#### 2. Charging Operation:

- a. Applying a voltage across the plates will pump electrons out of negative battery terminal.
- b. The electrons then collect on the lower plate while electrons are drawn away from the upper plate.
- c. The top plate will reach a charge  $+Q$ , while the lower plate will reach a negative charge  $-Q$ .
- d. This continues until equilibrium is reached.
- e. The electric field between the plates will remain even after the battery has been removed.

#### 3. Definitions and Units

Capacitance ( $C$ ) = ratio of electrical charge ( $Q$ ) to voltage ( $V$ )

Units: 1 farad (F) = 1 coulomb/volt

4. Capacitors Formulas: (Note: capacitor will have constant capacitance)

$$C = \frac{Q}{V} = \frac{dQ/dt}{dV/dt} = \frac{I}{dV/dt}$$

$$\rightarrow I = C \frac{dV}{dt}$$

5. Symbols

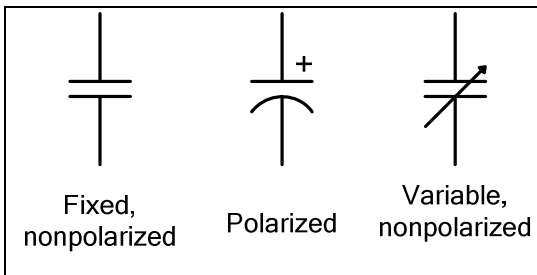


Figure 2. Symbols for capacitors.

## II. RC Circuit

Example: Find the dynamic model of the voltage across the capacitor,  $V_{be}$ .

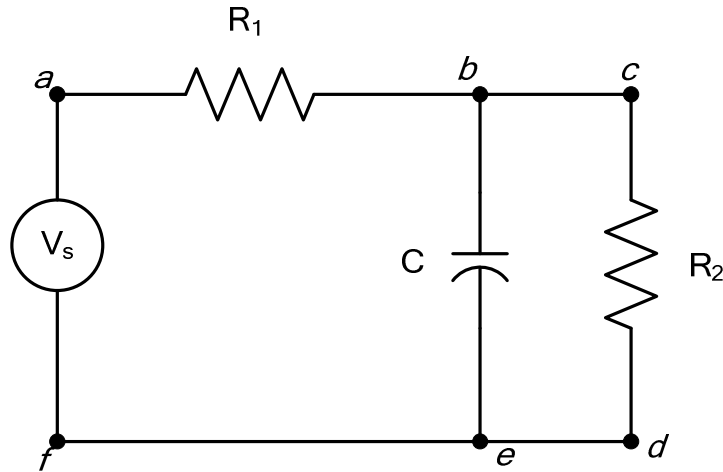


Figure 3. An RC circuit.

Solution:

Applying Kirchoff's Laws:

$$\begin{aligned}V_s &= V_{ab} + V_{be} \\V_{cd} &= V_{be} \\I_{ab} &= I_{be} + I_{cd}\end{aligned}$$

Next, apply Ohm's law and the capacitor equation:

$$\frac{V_{ab}}{R_1} = C \frac{dV_{be}}{dt} + \frac{V_{cd}}{R_2}$$

Put everything in terms of  $V_{be}$ ,  $V_s$ ,  $R_1$ ,  $R_2$  and  $C$ :

$$\frac{V_s - V_{be}}{R_1} = C \frac{dV_{be}}{dt} + \frac{V_{be}}{R_2}$$

which can be rearrange into the standard form:

$$\left( \frac{C}{\frac{1}{R_1} + \frac{1}{R_2}} \right) \frac{dV_{be}}{dt} + V_{be} = \left( \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} \right) V_s$$

### Reference:

Paul Scherz, **Practical Electronics for Inventors 2<sup>nd</sup> Edition**, McGraw Hill, New York, 2007.